

Practical 6
Logic Gates and Adders

Part A

Objective

Understand various logic gates


1. Complete questions below	
A	<div>Draw a transistor level circuit diagram and truth table for a OR Gate which consists of NOR and NOT gates</div> <div>(5 marks)</div>
B	<div>Draw a transistor level circuit diagram and truth table for a XOR Gate which consists of NAND and OR gates</div> <div>(6 marks)</div>
C	<div>Draw a transistor level circuit diagram and truth table for a AND Gate which consists of NAND and NOT gates</div> <div>(5 marks)</div>
D	<div>De Morgan's Law can be expressed as "the negation of a conjunction is the disjunction of the negations" and that "the negation of a disjunction is the conjunction of the negations". Prove, using a truth table, that:</div> <div style="text-align: center;">$\neg(A \wedge B) = \neg A \vee \neg B$</div> <div>(14 marks)</div>
E	Draw a logic Gate diagram for De Morgan's Law.
F	Draw a Transistor Gate diagram for De Morgan's Law. Why is this an important law.

Practical 6

Logic Gates and Adders

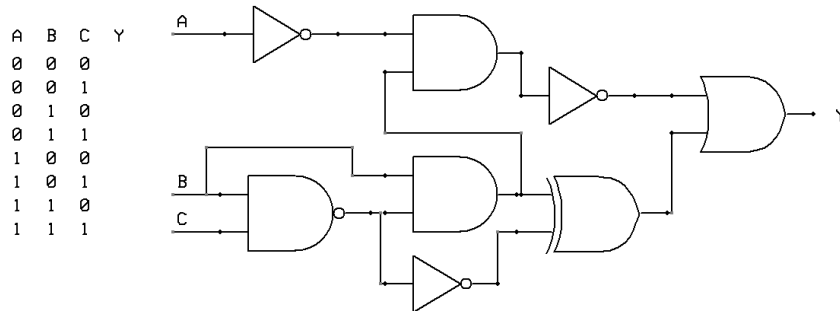2. Complete questions below

Using logic.ly construct the following Circuit using NAND and NOT Gates (With a Light at Output) and complete Truth Tables



Hand up this practical report at the end of session and ensure it has been checked

Student Name		Student Number	
Date		Checked	
Group	A / B		